

13.2 Linia transmisi di regime sinusoidal.

$$(3) \begin{cases} i(x, t) = I\sqrt{2} \sin(\omega t + \varphi_i) \\ u(x, t) = U\sqrt{2} \sin(\omega t + \varphi_u) \end{cases}$$

$$(4) \begin{cases} \underline{I} = \underline{I} e^{j\varphi_i} \\ \underline{U} = \underline{U} e^{j\varphi_u} \end{cases}$$

$$\begin{cases} \frac{\partial \underline{U}}{\partial x} = R' \cdot \underline{I} + j\omega L' \cdot \underline{I} \\ \frac{\partial \underline{I}}{\partial x} = G' \cdot \underline{U} + j\omega C' \cdot \underline{U} \end{cases}$$

$$\frac{\partial^2 \underline{U}}{\partial x^2} = (R' + j\omega L') \cdot \frac{\partial \underline{I}}{\partial x}$$

$$\frac{\partial^2 \underline{U}}{\partial x^2} = (R' + j\omega L') (G' + j\omega C') \cdot \underline{U}$$

Notăm $(R' + j\omega L')(G' + j\omega C') = \gamma^2$ - parametru line-
 ric de propagare

$$\begin{cases} \frac{\partial u}{\partial x} - \gamma^2 u = 0 \\ \frac{\partial I}{\partial x} - \gamma^2 \cdot I = 0. \end{cases}$$

$$u = A e^{j\gamma x} + B e^{-j\gamma x}$$

$$I = \frac{\partial u}{\partial x} \cdot \frac{1}{R' + j\omega L'}$$

$$= \frac{\gamma A e^{j\gamma x} - \gamma B e^{-j\gamma x}}{R' + j\omega L'}$$

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

$$\underline{I} = \frac{\sqrt{G' + j\omega C'}}{j\omega L' + R'} \cdot A e^{j\gamma x} - B e^{-j\gamma x}$$

$$= \frac{1}{Z_0} (A e^{j\gamma x} - B e^{-j\gamma x})$$

Z_0 impedanță caracteristică complexă