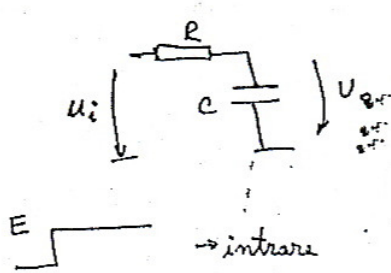


SEMINAR - 1



$$u_o(t) = U(\infty) + [U(0) - U(\infty)] \cdot e^{-\frac{t}{\tau}}$$

$$[\Omega] \cdot [F] = [sec]$$

$$\frac{[H]}{[R]} = [sec]$$

$$u_o(0) = 0 \text{ (capacitatea era descărcată)}$$

$$U(\infty) = E$$

$$\tau = RC$$

Met. I

$$\frac{dx}{dt} + px = q \quad x(0)$$

$$\tau = \frac{1}{p}$$

$$x(\infty) = \frac{q}{p}$$

$$u_o = R u_i - R \cdot I$$

$$I = C \frac{du_o}{dt}$$

$$\frac{du_o}{dt} + \frac{1}{RC} u_o = \frac{u_i}{RC}$$

$$\tau = RC$$

$$u_o(\infty) = E$$


Met. II

$$U_o(\Delta) = U_i(\Delta) \cdot \frac{\frac{1}{\Delta C}}{R + \frac{1}{\Delta C}} = \frac{E}{\Delta(1+RC\Delta)} = E \left[\frac{A}{s} + \frac{B}{1+RC\Delta} \right]$$

$$= \frac{E}{s} - \frac{E}{\Delta + \frac{1}{RC}}$$

$$\mathcal{L}(e^{-at}) = \frac{1}{\Delta + a}$$
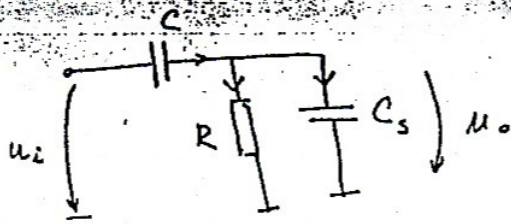
$$\Rightarrow u_o(t) = E(1 - e^{-\frac{t}{\tau}})$$



Calculer et. de timp.

$$u_o' = R \left[C \frac{d(u_i - u_o)}{dt} - C_s \frac{du_o}{dt} \right]$$

$$= \frac{du_o}{dt} + u_o \frac{1}{R(C+C_s)} = 0 \quad (u_i \text{ e constantă, derivata e } 0)$$

$$\tau = R(C+C_s)$$

$$U_o(\infty) = 0$$

