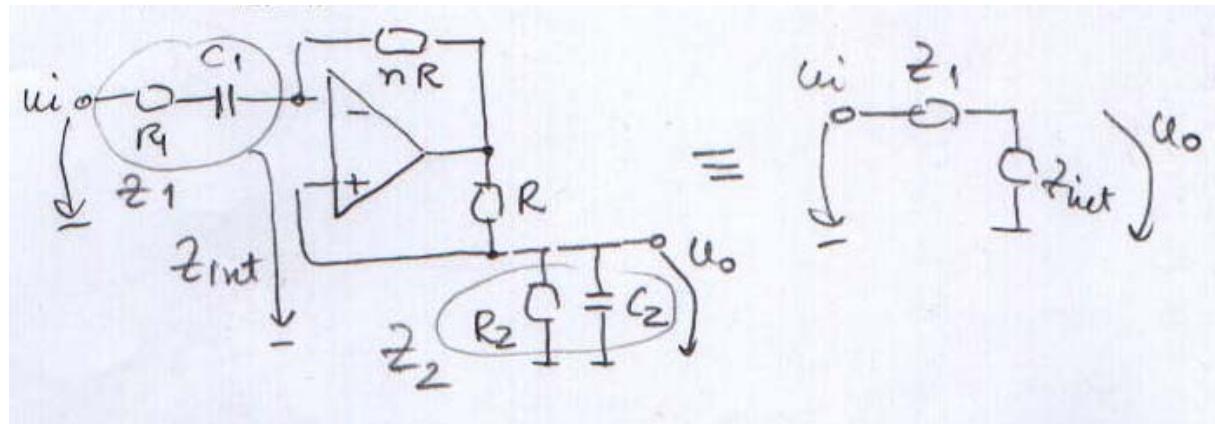


Implementarea filtrelor cu convertor de impedanta negative (CIN)

Exemplu de FTB cu CIN

Structura prezentata utilizeaza un CIN avand cuplat pe iesire un grup RC paralel. Se utilizeaza rezultatul obtinut la CIN pentru impedanta de intrare.

$$Z_{int} = -\frac{z_2}{k}, \quad k = \frac{R}{nR} = \frac{1}{n}$$



Calculez $H(s)$ si parametrii filtrului trece banda FTB.

$$H(s) = \frac{u_o(s)}{u_i(s)} = \frac{z_{int}}{z_1 + z_{int}} = \frac{-nz_2}{z_1 - z_2 n}$$

$$\text{dar } z_1 = R_1 + \frac{1}{sC_1} \quad \text{si} \quad z_2 = \frac{R_2 \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{R_2}{sR_2 C_2 + 1}$$

$$H(s) = \frac{\frac{-nR_2}{sR_2 C_2 + 1}}{R_1 + \frac{1}{sC_1} - \frac{nR_2}{sR_2 C_2 + 1}} = \frac{-nR_2 C_1 s}{R_1 C_1 s(sR_2 C_2 + 1) + sR_2 C_2 + 1 - nsC_1 R_2} =$$

$$= \frac{-\frac{n}{R_1 C_2} s}{s^2 + s(\frac{R_1 C_1 + R_2 C_2 - nC_1 R_2}{R_1 C_1 R_2 C_2}) + \frac{1}{R_1 C_1 R_2 C_2}}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$


$$\frac{\omega_0}{Q} = \frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} - \frac{n}{R_1 C_2}$$

$$\frac{\omega_0}{Q} H_0 = -\frac{n}{R_1 C_2}$$

$$BT = \frac{\omega_0}{Q}$$

Implementarea filtrelor cu giratoare

Exemplu de FRB cu girator modificat

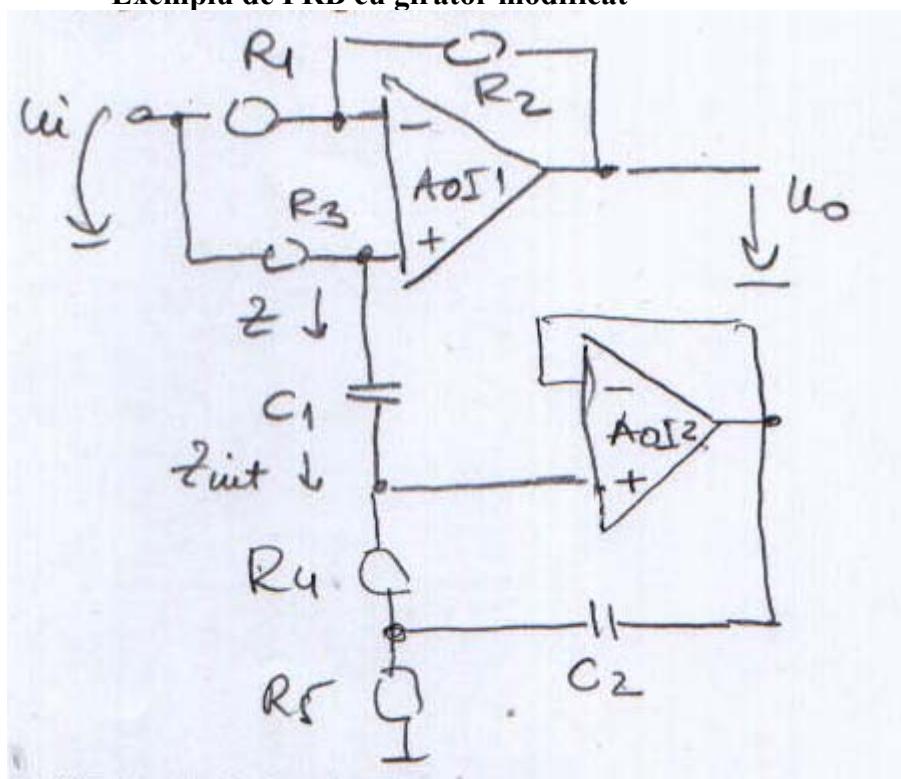


Pentru AOI1 functia de transfer este urmatoarea:

$$H(s) = -\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1}\right) \frac{Z}{R_3 + Z}$$

Calculez Z ptr AOI2

$$Z = \frac{1}{sC_1} + Z_{int}$$

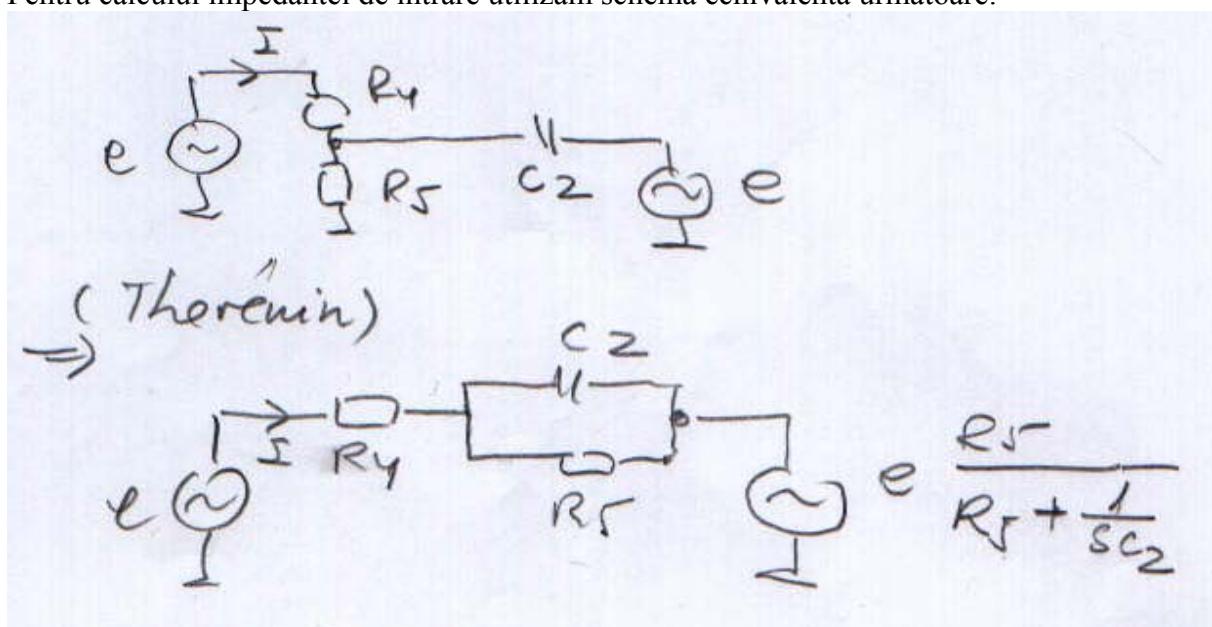Pentru calculul impedantei de intrare utilizam schema echivalenta urmatoare:



Notite

$$\begin{aligned}
 Z_{\text{int}} &= \frac{e}{I} = \frac{1}{(1 - \frac{R_5}{R_5 + \frac{1}{sC_2}}) (R_4 + \frac{1}{sC_2} // R_5)} = \\
 &= \frac{R_2 \frac{1}{sC_2}}{R_4 + \frac{R_5 + \frac{1}{sC_2}}{R_5 + \frac{1}{sC_2}}} = sC_2 \left[R_4 \left(R_5 + \frac{1}{sC_2} \right) + \frac{R_5}{sC_2} \right] = R_4 R_5 sC_2 + (R_4 + R_5) \\
 &\quad \frac{R_5 + \frac{1}{sC_2}}{R_5 + \frac{1}{sC_2}}
 \end{aligned}$$

Impedanta de intrare este o bobina in serie cu o rezistenta In aceste conditii:

$$Z = \frac{1}{sC_1} + R_4 R_5 sC_2 + (R_4 + R_5)$$

Inlocuind in expresia functiei de transfer abtinem:

$$H(s) = \frac{z - \frac{R_3 R_4}{R_1}}{R_3 + z} = \frac{R_4 R_5 C_1 C_2 s^2 + sC_1 (R_4 + R_5) + 1 - \frac{R_3 R_2}{R_1} sC_1}{R_4 R_5 C_1 C_2 s^2 + sC_1 (R_4 + R_5) + 1 + sC_1 R_3}$$

Analiză:

Dacă: $R_4 + R_5 = R_3 R_2 / R_1 \Rightarrow \text{FRB}$;


Dacă: $-(R_4 + R_5) + R_3 R_2 / R_1 = R_3 + R_4 + R_5$ adica $R_3 (R_2 / R_1 - 1) = 2(R_4 + R_5) \Rightarrow \text{FTT}$

Implementarea filtrelor cu multiplicatoare

Simbolul general al unui multiplicator este urmatorul:

$$\begin{array}{c} u_x \\ u_y \end{array} \xrightarrow{\boxed{\times}} u_o = \frac{u_x u_y}{k} \quad ; \quad [k]_{\text{si}} = 1 \text{ Volts}$$

Exemplu de FTJ realizat cu multiplicator

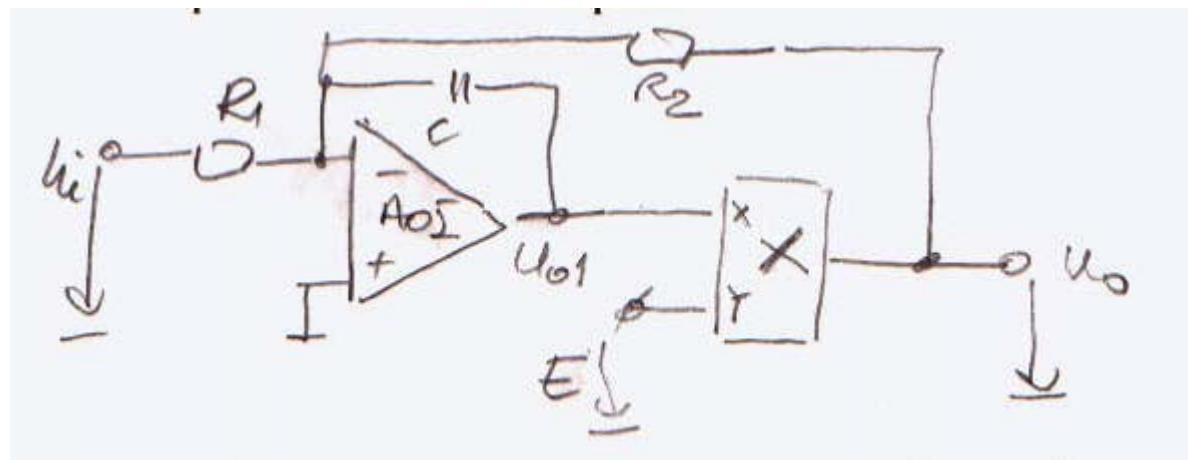

Notite

$$\text{Avem: } u_0(s) = U_{01}E/K$$


$$u_{01}(s) = -\frac{1}{R_1 C s} u_i(s) - \frac{1}{R_2 C s} u_0 \Rightarrow$$

$$u_0(s) = -\frac{E}{k} \left(\frac{1}{R_1 C s} u_i(s) + \frac{1}{R_2 C s} u_0(s) \right) \Rightarrow$$

$$H(s) = \frac{-\frac{E}{k} \frac{1}{R_1 C s}}{1 + \frac{E}{k} \frac{1}{R_2 C s}} = \frac{-\frac{E}{k} \frac{1}{R_1 C}}{s + \frac{E}{k} \frac{1}{R_2 C}} \Rightarrow \text{FTJ de ordinul unu}$$

$$H_0 = \left(-\frac{E}{k} \frac{1}{R_1 C} \right) \cdot \frac{1}{\frac{E}{k} \frac{1}{R_2 C}} = -\frac{R_2}{R_1}$$

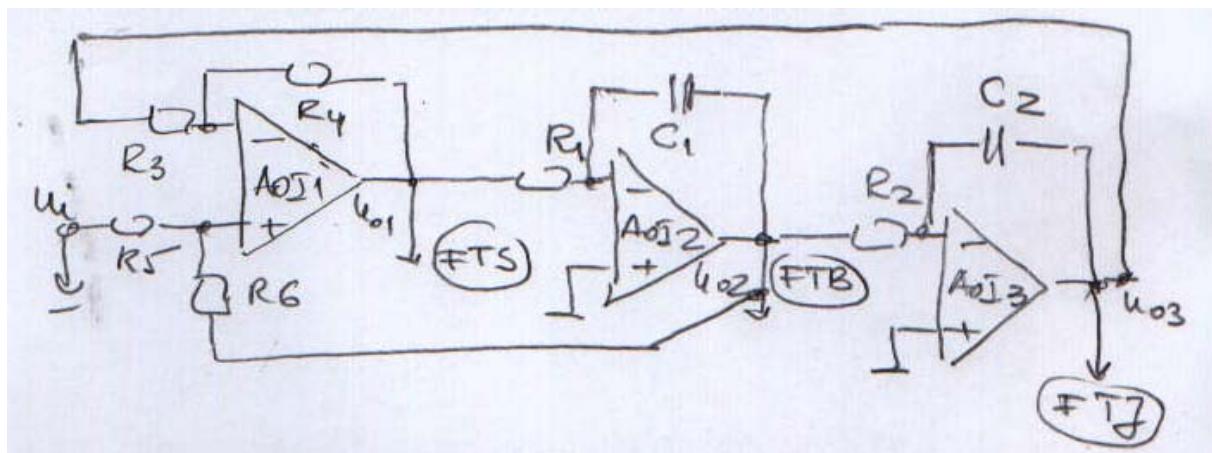Implementarea filtrelor prin metoda variabilelor de stare



Observam ca amplificatoarele AOI2 si AOI3 indeplinesc functia de filtru trece jos de ordinul unu in configuratie de amplificator inversor, iar AOI1 este un amplificator diferential cu sumare pe borna neinversoare. In aceste conditii functiile de transfer asociate acestor structuri au expresiile:

$$u_{02} = u_{01} \left(-\frac{sC_1}{R_1} \right) = -u_{01} \frac{1}{R_1 C_1 s} \quad (\text{ec1})$$

$$u_{03} = -u_{02} \frac{1}{R_2 C_2 s} \quad (\text{ec.2})$$

$$u_{01} = u_{03} \left(-\frac{R_4}{R_3} \right) + u_i \frac{R_6}{R_5 + R_6} \left(1 + \frac{R_4}{R_3} \right) + u_{02} \frac{R_5}{R_5 + R_6} \left(1 + \frac{R_4}{R_3} \right)$$

Demonstrez ca la iesirea u_{01} se obtine FTS

$$u_{01} = \left(-\frac{R_4}{R_3} \right) \left(-\frac{1}{R_1 C_1 s} \right) \left(-\frac{1}{R_1 C_1 s} \right) u_{01} + u_i \frac{R_6}{R_5 + R_6} \left(1 + \frac{R_4}{R_3} \right) - u_{01} \frac{R_5}{R_5 + R_6} \frac{1}{R_1 C_1 s}$$

Notite

$$H_1(s) = \frac{u_{01}(s)}{u_i(s)} = \frac{\frac{R_6}{R_5 + R_6} \left(1 + \frac{R_4}{R_3}\right)}{1 + \frac{R_4}{R_3} \frac{1}{R_1 C_1 R_2 C_2 s^2} + \frac{R_5}{R_6 + R_5} \frac{1}{R_1 C_1 s}}$$

Caz particular :

$$R_3 = R_4 = R_5 = R_6 = R; \quad R_1 C_1 = \tau_1; \quad R_2 C_2 = \tau_2$$


$$H_1(s) = \frac{1}{1 + \frac{1}{\tau_1 \tau_2 s^2} + \frac{1}{2\tau_1 s}} = \frac{\frac{1}{2}s^2}{s^2 + \frac{\tau_2}{2\tau_1} s + \frac{1}{\tau_1 \tau_2}}$$

=> FTS avand urmatorii parametrii:

$$\omega_0 = \sqrt{\frac{1}{\tau_1 \tau_2}}; \quad H_0 = \frac{1}{2};$$

$$\frac{\omega_0}{Q} = \frac{\tau_2}{2\tau_1} \Rightarrow Q = \frac{2\tau_1}{\tau_2} \sqrt{\frac{1}{\tau_1 \tau_2}} = \sqrt{\frac{4\tau_1^2}{\tau_1 \tau_2^3}} = \sqrt{\frac{4\tau_1}{\tau_2^3}}$$

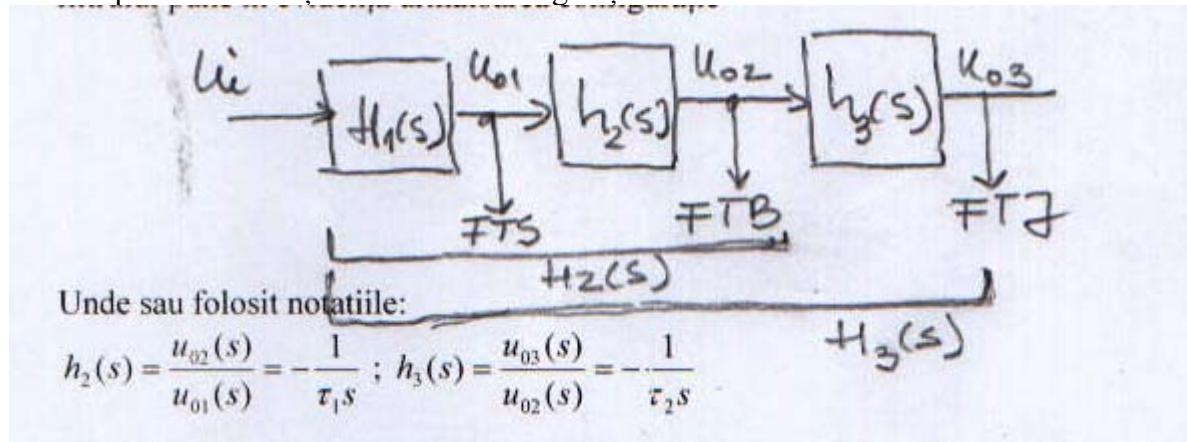Demonstrez ca la iesirea u_{02} si u_{03} se obtine un **FTB** respectiv **FTJ**. Structura filtrului pune in evidenta urmatoarea configuratie:



{Unde sau folosit notatiile:

$$h_2(s) = \frac{u_{02}(s)}{u_{01}(s)} = -\frac{1}{\tau_1 s}; \quad h_3(s) = \frac{u_{03}(s)}{u_{02}(s)} = -\frac{1}{\tau_2 s} \}$$

Functiile globale ale filtrelor obtinute sunt:

Notite

$$H_2(s) = \frac{u_{02}(s)}{u_i(s)} = H_1(s)h_2(s) = \frac{-\frac{1}{2\tau_1}s}{s^2 + \frac{\tau_2}{2\tau_1}s + \frac{1}{\tau_1\tau_2}} \quad (\text{FTB})$$

$$H_3(s) = \frac{u_{03}(s)}{u_i(s)} = H_2(s)h_3(s) = \frac{\frac{1}{2\tau_1\tau_2}}{s^2 + \frac{\tau_2}{2\tau_1}s + \frac{1}{\tau_1\tau_2}} \quad (\text{FTJ})$$