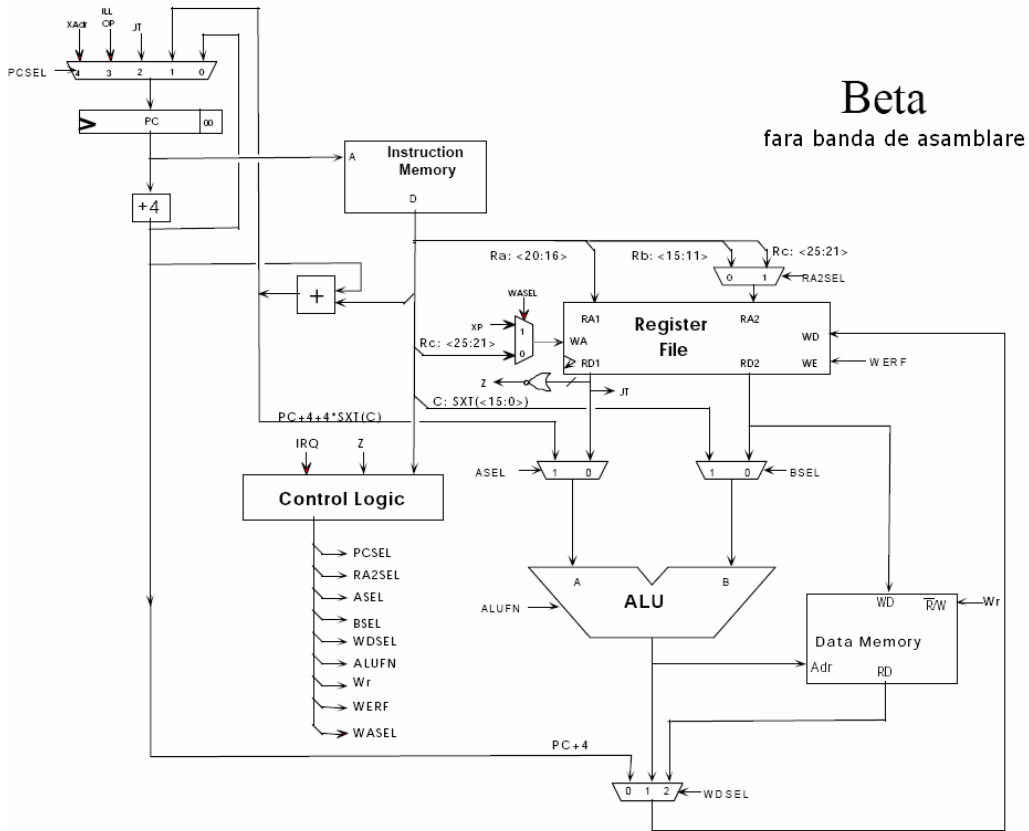


ANEXA la Cursul CN2_2

Procesorul RISC (Beta, fara banda de asamblare) (<http://6004.csail.mit.edu/>)




Logica de comand/control:

	<i>OP</i>	<i>OPC</i>	<i>LD</i>	<i>ST</i>	<i>JMP</i>	<i>BEQ</i>	<i>BNE</i>	<i>LDR</i>	<i>llop</i>	<i>trap</i>
<i>ALUFN</i>	F(op)	F(op)	"+"	"+"	—	—	—	"A"	—	—
<i>WERF</i>	1	1	1	0	1	1	1	1	1	1
<i>BSEL</i>	0	1	1	1	—	—	—	—	—	—
<i>WDSEL</i>	1	1	2	—	0	0	0	2	0	0
<i>WR</i>	0	0	0	1	0	0	0	0	0	0
<i>RA2SEL</i>	0	—	—	1	—	—	—	—	—	—
<i>PCSEL</i>	0	0	0	0	2	Z ? 1 : 0	Z ? 0 : 1	0	3	4
<i>ASEL</i>	0	0	0	0	—	—	—	1	—	—
<i>WASEL</i>	0	0	0	—	0	0	0	0	1	1

β Instruction Formats


Operate Class: Summary

 

OP(Ra,Ra,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{Reg}[Rb]$

Opcodes: **ADD** (plus), **SUB** (minus), **MUL** (multiply), **DIV** (divided by)
AND (bitwise and), **OR** (bitwise or), **XOR** (bitwise exclusive or)
CMPEQ (equal), **CMPLT** (less than), **CMPLE** (less than or equal) [result = 1 if true, 0 if false]
SHL (left shift), **SHR** (right shift w/o sign extension), **SRA** (right shift w/ sign extension)


Register	Symbol	Usage
R31	R31	Always zero
R30	XP	Exception pointer
R29	SP	Stack pointer
R28	LP	Linkage pointer
R27	BP	Base of frame pointer

 

OPC(Ra,literal,Rc): $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{SEXT}(\text{literal})$

Opcodes: **ADD C** (plus), **SUB C** (minus), **MUL C** (multiply), **DIV C** (divided by)
AND C (bitwise and), **OR C** (bitwise or), **XOR C** (bitwise exclusive or)
CMPEQ C (equal), **CMPLT C** (less than), **CMPLE C** (less than or equal) [result = 1 if true, 0 if false]
SHL C (left shift), **SHR C** (right shift w/o sign extension), **SRA C** (right shift w/ sign extension)


Other:

 

LD(Ra,literal,Rc): $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{Reg}[Ra] + \text{SEXT}(\text{literal})]$
ST(Rc,literal,Ra): $\text{Mem}[\text{Reg}[Ra] + \text{SEXT}(\text{literal})] \leftarrow \text{Reg}[Rc]$
JMP(Ra,Rc): $\text{Reg}[Rc] \leftarrow \text{PC} + 4; \text{PC} \leftarrow \text{Reg}[Ra]$
BEQ/BF(Ra,label,Rc): $\text{Reg}[Rc] \leftarrow \text{PC} + 4; \text{if } \text{Reg}[Ra] = 0 \text{ then } \text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$
BNE/BT(Ra,label,Rc): $\text{Reg}[Rc] \leftarrow \text{PC} + 4; \text{if } \text{Reg}[Ra] \neq 0 \text{ then } \text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SEXT}(\text{literal})$
LDR(Ra,label,Rc): $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SEXT}(\text{literal})]$


Opcode Table: (*optional opcodes)

5:3	2:0	000	001	010	011	100	101	110	111
000									
001									
010									
011	LD	ST		JMP		BEQ	BNE	LDR	
100	ADD	SUB	MUL*	DIV*	CMPEQ	CMPLT	CMPLE		
101	AND	OR	XOR		SHL	SHR	SRA		
110	ADD C	SUB C	MUL C*	DIV C*	CMPEQ C	CMPLT C	CMPLE C		
111	AND C	OR C	XOR C		SHL C	SHR C	SRA C		

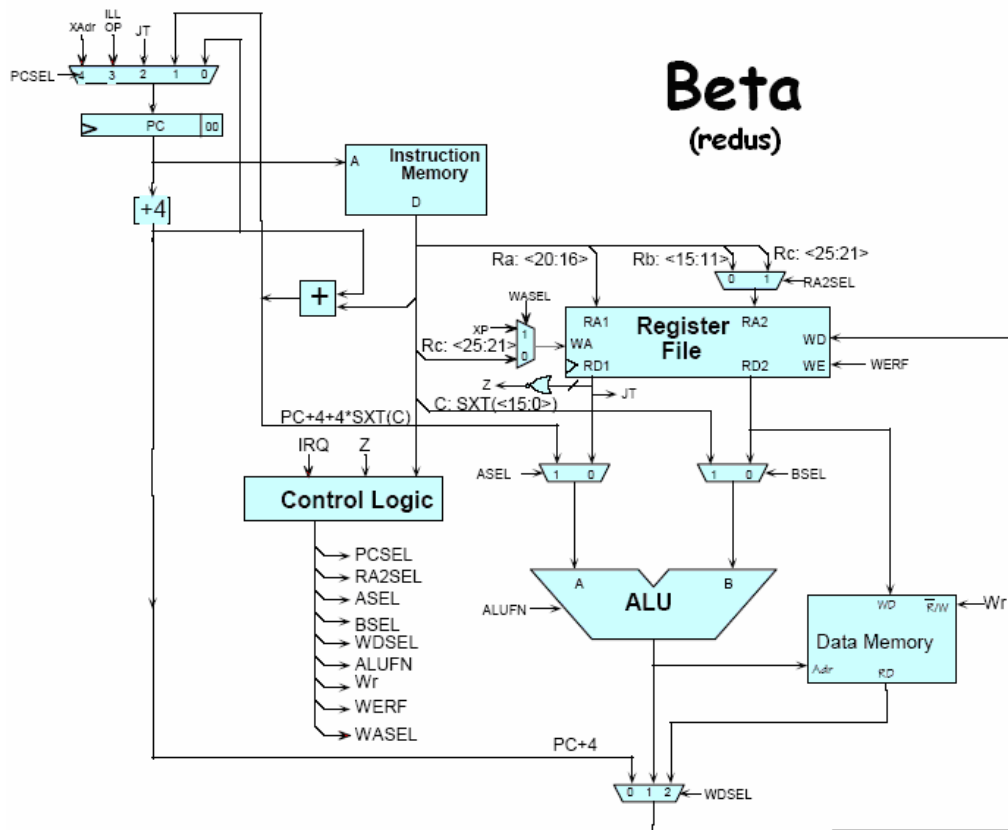

Beta (reduz)

Divide and conquer...

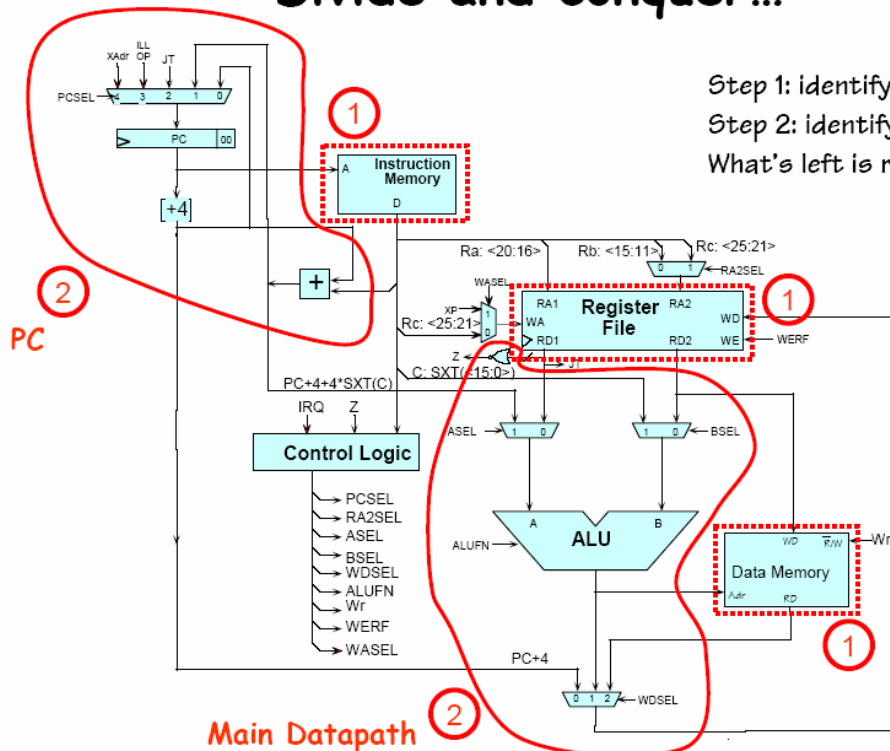

Step 1: identify memories
 Step 2: identify datapaths
 What's left is random logic...

Beta Module Hierarchy

- beta
 - control [random logic]
 - regfile [memory]
 - pc [datapath]
 - datapath
 - dp_misc [datapath]
 - dp_alu
 - dp_addsub [datapath]
 - dp_boole [datapath]
 - dp_shift [datapath]
 - dp_cmp [datapath]
 - dp_mux [datapath]
 - dp_wdata [datapath]

```
// Beta PC logic
module pc(clk,reset,pcsel,offset,jump_addr,branch_addr,pc,pc_plus_4);
  input clk;
  input reset; // forces PC to 0x80000000
  input [2:0] pcsel; // selects source of next PC
  input [15:0] offset; // inst[15:0]
  input [31:0] jump_addr; // from Reg[RA], used in JMP instruction
  output [31:0] branch_addr; // send to datapath for LDR instruction
  output [31:0] pc; // used as address for instruction fetch
  output [31:0] pc_plus_4; // saved in regfile during branches,JMP,traps

  reg [31:0] pc;
  wire [30:0] pcinc;
  wire [31:0] npc;

  // the Beta PC increments by 4, but won't change supervisor bit
  assign pcinc = pc + 4;
  assign pc_plus_4 = {pc[31],pcinc};

  // branch address = PC + 4 + 4*sxt(offset)
  assign branch_addr = {1'b0, pcinc +
  {{13{offset[15]}},offset[15:0],2'b00}};

  assign npc = reset ? 32'h80000000 :
  (pcsel == 0) ? {pc[31],pcinc} : // normal
  (pcsel == 1) ? {pc[31],branch_addr[30:0]} : // branch
  (pcsel == 2) ? {pc[31] & jump_addr[31],jump_addr[30:0]}://jump
```

```

        (pcsel == 3) ? 32'h80000004 :
        (pcsel == 4) ? 32'h80000008 :           // illop, trap
        32'hXXXXXXXX;                          // catch errors...

    // pc register, pc[31] is supervisor bit and gets special treatment
    always @(posedge clk) pc <= npc;
endmodule

```

```

// 2-read, 1-write 32-location register file
module regfile(ra1,rd1,ra2,rd2,clk,werf,wa,wd);
    input [4:0] ra1;           // address for read port 1 (Reg[RA])
    output [31:0] rd1;        // read data for port 1
    input [4:0] ra2; // address for read port 2 (Reg[RB], Reg[RC] for ST)
    output [31:0] rd2;        // read data for port 2
    input clk;
    input werf;               // write enable, active high
    input [4:0] wa;           // address for write port (Reg[RC])
    input [31:0] wd;          // write data

    reg [31:0] registers[31:0]; // the register file itself

    // read paths are combinational
    // logic to ensure R31 reads as zero is in main datapath
    assign rd1 = registers[ra1];
    assign rd2 = registers[ra2];

    // write port is active only when WERF is asserted
    always @(posedge clk)
        if (werf) registers[wa] <= wd;
endmodule

```

```

module dp_addsub(fn,alu_a,alu_b,result,n,v,z);
    input fn;                 // 0 for add, 1 for subtract
    input [31:0] alu_a;       // A operand
    input [31:0] alu_b;       // B operand
    output [31:0] result;     // result
    output n,v,z;             // condition codes computed from result

    reg n,v,z;
    reg [31:0] result;

    always @(fn or alu_a or alu_b) begin: ripple
        integer i;           // FOR loop index, not in hardware
        reg cin,p,g;         // expanded at compile time into many signals
        reg [31:0] xb;       // hold's complement of ALU_B during subtract

        // simple ripple-carry adder for now
        xb = fn ? ~alu_b : alu_b; // a - b == a + ~b + 1
        cin = fn;                // carry in is 0 for add, 1 for sub
        // remember: this FOR is expanded at *compile* time
        for (i = 0; i < 32; i = i + 1) begin
            p = alu_a[i] ^ xb[i]; // carry propagate
            g = alu_a[i] & xb[i]; // carry generate

```

```

        result[i] = p ^ cin;
        cin = g | (p & cin); // carry into next stage
    end

    n = result[31]; // negative
    z = ~|result; // zero
    v = (alu_a[31] & xb[31] & !n) | (~alu_a[31] & ~xb[31] & n); //overflow
end
endmodule

```

```

// fn == 2'b01: eq (Z)
// fn == 2'b10: lt (N ^ V)
// fn == 2'b11: le (Z | (N ^ V))
// result is 1 if comparison is true, 0 otherwise
module dp_cmp(fn,n,v,z,result);
    input [1:0] fn;
    input n,v,z;
    output [31:0] result;

    assign result = {31'b0,(fn[0] & z) | (fn[1] & (n ^ v))};
endmodule

```

```

// fn == 2'b00: logical shift left
// fn == 2'b01: logical shift right
// fn == 2'b11: arithmetic shift right
module dp_shift(fn,alu_a,alu_b,result);
    input [1:0] fn;
    input [31:0] alu_a;
    input [4:0] alu_b;
    output [31:0] result;

    wire sin;
    reg [31:0] u,result;
    wire [31:0] v,w,x,y,z;

    assign sin = fn[1] & alu_a[31];

    // assign u = fn[0] ? alu_a[0:31] : alu_a[31:0]
    always @(fn[0] or alu_a) begin: loopA
        integer i;
        for (i = 0; i < 32; i = i + 1)
            u[i] = fn[0] ? alu_a[31 - i] : alu_a[i];
    end

    assign v = alu_b[4] ? {u[15:0],{16{sin}}} : u[31:0];
    assign w = alu_b[3] ? {v[23:0],{8{sin}}} : v[31:0];
    assign x = alu_b[2] ? {w[27:0],{4{sin}}} : w[31:0];
    assign y = alu_b[1] ? {x[29:0],{2{sin}}} : x[31:0];
    assign z = alu_b[0] ? {y[30:0],sin} : y[31:0];

    // assign result = fn[0] ? z[0:31] : z[31:0]
    always @(fn[0] or z) begin: loopB
        integer i;

```

```

        for (i = 0; i < 32; i = i + 1)
            result[i] = fn[0] ? z[31 - i] : z[i];
    end
endmodule

```

```

// fn is truth table for boolean operation:
// AND: fn = 4'b1000
// OR:  fn = 4'b1110
// XOR: fn = 4'b0110
// A:   fn = 4'b1010
module dp_boole(fn,alu_a,alu_b,result);
    input  [3:0] fn;
    input  [31:0] alu_a,alu_b;
    output [31:0] result;

    reg [31:0] result;

    always @(fn or alu_a or alu_b) begin: bits
        integer i;
        for (i = 0; i < 32; i = i + 1) begin
            result[i] = alu_b[i] ? (alu_a[i] ? fn[3] : fn[2]) :
                (alu_a[i] ? fn[1] : fn[0]);
        end
    end
endmodule

```

```

module dp_mux(sel,addsub,boole,shift,cmp,alu);
    input  [1:0] sel;
    input  [31:0] addsub;
    input  [31:0] boole;
    input  [31:0] shift;
    input  [31:0] cmp;
    output [31:0] alu;

    assign alu = (sel == 2'b00) ? addsub :
        (sel == 2'b01) ? boole :
        (sel == 2'b10) ? shift :
        (sel == 2'b11) ? cmp :
        32'hXXXXXXXX;
endmodule

```

```

module dp_misc(rd1zero,rd2zero,asel,bsel,inst,rd1,rd2,branch_addr,
    alu_a,alu_b,jump_addr,mem_wr_data,z);
    input rd1zero;           // RA == R31, so treat RD1 as 0
    input rd2zero;           // RB/RC == R31, so treat RD2 as 0
    input asel;              // select A operand for ALU
    input bsel;              // select B operand for ALU
    input [15:0] inst;       // constant field from instruction
    input [31:0] rd1;        // Reg[RA] from register file
    input [31:0] rd2;        // Reg[RB] from register file (Reg[RC] for ST)
    input [31:0] branch_addr; // PC + 4 + 4*sxt(inst[15:0])

```

```

output [31:0] alu_a;      // A input to ALU
output [31:0] alu_b;      // B input to ALU
output [31:0] jump_addr; // jump address (from Reg[RA])
output [31:0] mem_wr_data; // data memory write data
output z;                // true if Reg[RA] is zero, used during branches

// R31 reads as 0, so make that adjustment here
assign jump_addr = rd1zero ? 32'b0 : rd1;
assign mem_wr_data = rd2zero ? 32'b0 : rd2;

assign z = ~|jump_addr;
assign alu_a = asel ? branch_addr : jump_addr;
assign alu_b = bsel[0] ? {{16{inst[15]}},inst[15:0]} : mem_wr_data;
endmodule

```

```

module dp_alu(alufn,alu_a,alu_b,alu);
input [5:0] alufn;
input [31:0] alu_a;
input [31:0] alu_b;
output [31:0] alu;

wire [31:0] addsub;
wire [31:0] boole;
wire [31:0] shift;
wire [31:0] cmp;
wire alu_n;
wire alu_v;
wire alu_z;

// the four functional units
dp_addsub alu1(alufn[0],alu_a,alu_b,addsub,alu_n,alu_v,alu_z);
dp_boole alu4(alufn[3:0],alu_a,alu_b,boole);
dp_shift alu3(alufn[1:0],alu_a,alu_b[4:0],shift);
dp_cmp alu2(alufn[2:1],alu_n,alu_v,alu_z,cmp);

// 4-to-1 mux selects alu output from functional units
dp_mux alu5(alufn[5:4],addsub,boole,shift,cmp,alu);
endmodule

```

```

module dp_wdata(wdsel,pc_plus_4,alu,mem_data,wdata);
input [1:0] wdsel;
input [31:0] pc_plus_4;
input [31:0] alu;
input [31:0] mem_data;
output [31:0] wdata;

assign wdata = wdsel[1] ? mem_data :
              wdsel[0] ? alu : pc_plus_4;
endmodule

```

```

module datapath(inst,rd1,rd2,pc_plus_4,branch_addr,mem_rd_data,
                rd1zero,rd2zero,asel,bsel,wdsel,alufn,
                wdata,mem_addr,jump_addr,mem_wr_data,z);
    input [15:0] inst;           // constant field from instruction
    input [31:0] rd1;           // Reg[RA] from register file
    input [31:0] rd2;           // Reg[RB] from register file (Reg[RC] for ST)
    input [31:0] pc_plus_4;     // incremented PC
    input [31:0] branch_addr;   // PC + 4 + 4*sxt(inst[15:0])
    input [31:0] mem_rd_data;   // memory read data (for LD)
    input rd1zero;              // RA == R31, so treat RD1 as 0
    input rd2zero;              // RB/RC == R31, so treat RD2 as 0
    input asel;                  // select A operand for ALU
    input bsel;                  // select B operand for ALU
    input [1:0] wdsel;           // select regfile write data
    input [5:0] alufn;           // operation to be performed by alu
    output [31:0] wdata;         // regfile write data (output of WDSEL mux)
    output [31:0] mem_addr;     // alu output, doubles as data memory address
    output [31:0] jump_addr;    // jump address (from Reg[RA])
    output [31:0] mem_wr_data;  // data memory write data (from Reg[RC])
    output z;                    // true if Reg[RA] is zero, used during branches

    wire [31:0] alu_a;           // A input to ALU
    wire [31:0] alu_b;           // B input to ALU

    // compute A and B inputs into alu, also Z bit for control logic
    dp_misc misc(rd1zero,rd2zero,asel,bsel,inst,rd1,rd2,branch_addr,
                alu_a,alu_b,jump_addr,mem_wr_data,z);

    // where all the heavy-lifting happens
    dp_alu alu(alufn,alu_a,alu_b,mem_addr);

    // select regfile write data from PC+4, alu output, and memory data
    dp_wdata wdata(wdsel,pc_plus_4,mem_addr,mem_rd_data,wdata);
endmodule

```

```

module control(reset,irq,supervisor,z,inst,
               alufn,asel,bsel,pcsel,ra2,rd1zero,rd2zero,wa,wdsel,werf,mem_we);
    input reset;                // active high
    input irq;                  // interrupt request, active high
    input supervisor;           // 1 for kernel-mode, 0 for user-mode
    input z;                    // Reg[RA] == 0, used for branch tests
    input [31:0] inst;           // current instruction
    output [5:0] alufn;          // selects ALU function
    output asel;                // selects ALU A operand
    output bsel;                // selects ALU B operand
    output [2:0] ptsel;         // selects next PC
    output [4:0] ra2;           // RB or RC
    output rd1zero;             // RA == 31
    output rd2zero;             // ra2 == 31
    output [4:0] wa;            // RC or XP
    output [1:0] wdsel;         // selects regfile write data
    output werf;                // regfile write enable
    output mem_we;              // memory write enable, active high

```

```

reg [15:0] ctl; // local
wire interrupt;

// interrupts enabled in user mode only
assign interrupt = irq & ~supervisor;

// control ROM
always @(inst or interrupt) begin
  if (interrupt)
    ctl = 16'bx_100_lxx_xxxxxx_00_0; // interrupt
  else case (inst[31:26])
    //          ppp      aaaaaa ww
    //          b ccc w   llllll dd
    //          t sss aab uuuuuu ss
    //          e eee sss ffffff ee x
    //          s lll eee nnnnnn ll w
    //          t 210 lll 543210 10 r
    default:  ctl = 16'bx_011_lxx_xxxxxx_00_0; // illegal opcode
    6'b011000: ctl = 16'bx_000_001_00xxx0_10_0; // LD
    6'b011001: ctl = 16'bx_000_x01_00xxx0_10_1; // ST
    6'b011011: ctl = 16'bx_010_0xx_xxxxxx_00_0; // JMP
    6'b011101: ctl = 16'b1_001_0xx_xxxxxx_00_0; // BEQ
    6'b011110: ctl = 16'b0_001_0xx_xxxxxx_00_0; // BNE
    6'b011111: ctl = 16'bx_000_010_011010_10_0; // LDR
    6'b100000: ctl = 16'bx_000_000_00xxx0_01_0; // ADD
    6'b100001: ctl = 16'bx_000_000_00xxx1_01_0; // SUB
    6'b100100: ctl = 16'bx_000_000_11x011_01_0; // CMPEQ
    6'b100101: ctl = 16'bx_000_000_11x101_01_0; // CMLPT
    6'b100110: ctl = 16'bx_000_000_11x111_01_0; // CMPLT
    6'b101000: ctl = 16'bx_000_000_011000_01_0; // AND
    6'b101001: ctl = 16'bx_000_000_011110_01_0; // OR
    6'b101010: ctl = 16'bx_000_000_010110_01_0; // XOR
    6'b101100: ctl = 16'bx_000_000_10xx00_01_0; // SHL
    6'b101101: ctl = 16'bx_000_000_10xx01_01_0; // SHR
    6'b101110: ctl = 16'bx_000_000_10xx11_01_0; // SRA
    6'b110000: ctl = 16'bx_000_001_00xxx0_01_0; // ADDC
    6'b110001: ctl = 16'bx_000_001_00xxx1_01_0; // SUBC
    6'b110100: ctl = 16'bx_000_001_11x011_01_0; // CMPEQC
    6'b110101: ctl = 16'bx_000_001_11x101_01_0; // CMLPTC
    6'b110110: ctl = 16'bx_000_001_11x111_01_0; // CMPLTC
    6'b111000: ctl = 16'bx_000_001_011000_01_0; // ANDC
    6'b111001: ctl = 16'bx_000_001_011110_01_0; // ORC
    6'b111010: ctl = 16'bx_000_001_010110_01_0; // XORC
    6'b111100: ctl = 16'bx_000_001_10xx00_01_0; // SHLC
    6'b111101: ctl = 16'bx_000_001_10xx01_01_0; // SHRC
    6'b111110: ctl = 16'bx_000_001_10xx11_01_0; // SRAC
  endcase
end

assign werf = ~ctl[0];
assign mem_we = !reset & ctl[0];
assign wdsel = ctl[2:1];
assign alufn = ctl[8:3];
assign bsel = ctl[9];
assign asel = ctl[10];
assign wa = ctl[11] ? 5'b11110 : inst[25:21];

```

```

    assign pcsel = ((ctl[14:12] == 3'b001) & (ctl[15] ^ z)) ? 3'b000 :
ctl[14:12];

    assign ra2 = ctl[0] ? inst[25:21] : inst[15:11];
    assign rd1zero = (inst[20:16] == 5'b11111);
    assign rd2zero = (ra2 == 5'b11111);
endmodule

```

```

module beta(clk,reset,irq,inst_addr,inst_data,
            mem_addr,mem_rd_data,mem_we,mem_wr_data);
    input clk;
    input reset;                // active high
    input irq;                  // interrupt request, active high
    output [31:0] inst_addr;    // address of instruction to be fetched
    input [31:0] inst_data;     // instruction returning from memory
    output [31:0] mem_addr;     // address of data word to be accessed
    input [31:0] mem_rd_data;   // read data returning from memory
    output mem_we;             // memory write enable, active high
    output [31:0] mem_wr_data;  // memory write data

    // internal signals
    wire [5:0] alufn;          // [control] selects ALU function
    wire asel;                // [control] selects ALU A operand
    wire [31:0] branch_addr;   // [pc] PC + 4 +
4*sxt(inst[15:0])
    wire bsel;                // [control] selects ALU B operand
    wire [31:0] jump_addr;     // [datapath] Reg[RA]
    wire [31:0] pc_plus_4;     // [pc] PC + 4
    wire [2:0] pcsel;         // [control] selects next PC
    wire [4:0] ra2;           // [control] RB or RC
    wire [31:0] rd1;          // [regfile] Reg[RA]
    wire rd1zero;            // [control] RA == 31
    wire [31:0] rd2;          // [regfile] Reg[ra2]
    wire rd2zero;            // [control] ra2 == 31
    wire [4:0] wa;            // [control] RC or XP
    wire [1:0] wdsel;         // [control] selects regfile write data
    wire werf;                // [control] regfile write enable
    wire [31:0] wdata;        // [datapath] regfile write data
    wire z;                   // [datapath] Reg[RA] == 0

    // control logic, reg file address generation
    control ctl(reset,irq,inst_addr[31],z,inst_data[31:0],
alufn,asel,bsel,pcsel,ra2,rd1zero,rd2zero,wa,wdsel,werf,mem_we);

    // program counter logic
    pc pc(clk,reset,pcsel,inst_data[15:0],jump_addr,branch_addr,
inst_addr,pc_plus_4);

    // register file
    regfile regfile(inst_data[20:16],rd1,ra2,rd2,clk,werf,wa,wdata);

    // datapath
    datapath
dp(inst_data[15:0],rd1,rd2,pc_plus_4,branch_addr,mem_rd_data,

```

```
        rd1zero,rd2zero,asel,bsel,wdsel,alufn,
        wdata,mem_addr,jump_addr,mem_wr_data,z);
endmodule
```

```
// Set time units to be nanoseconds.
`timescale 1ns/1ns

module main;
    reg clk,reset,irq;

    wire [31:0] inst_addr;
    wire [31:0] inst_data;
    wire [31:0] mem_addr;
    wire [31:0] mem_wr_data;
    wire [31:0] mem_rd_data;
    wire mem_we;

    reg [31:0] memory[1023:0];

    beta beta(clk,reset,irq,inst_addr,inst_data,
             mem_addr,mem_rd_data,mem_we,mem_wr_data);

    // main memory (2 async read ports, 1 sync write port)
    assign inst_data = memory[inst_addr[13:2]];
    assign mem_rd_data = memory[mem_addr[13:2]];
    always @(posedge clk)
        if (mem_we) memory[mem_addr[13:2]] <= mem_wr_data;

    always #5 clk = ~clk;

    initial begin
        $dumpfile("beta_checkoff.vcd");
        $dumpvars;
        $readmemh("beta_checkoff",memory);
        clk = 0; irq = 0; reset = 1;
        #10
        reset = 0;
        #3000 // 300 cycles
        $finish;
    end
endmodule
```