

Fig. 5.1 Block diagram of an OM system.

Fig.1 Schema bloc a microprocesorului

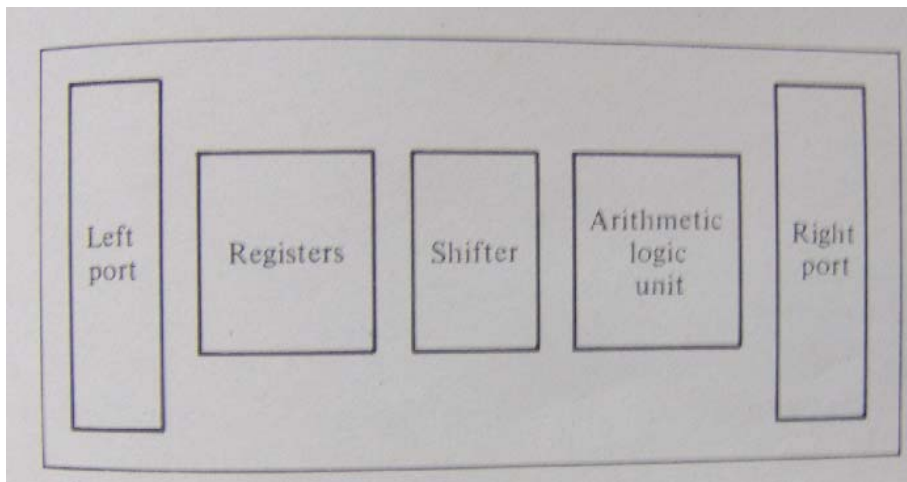


Fig. 2. Planul general al unitatii de executie

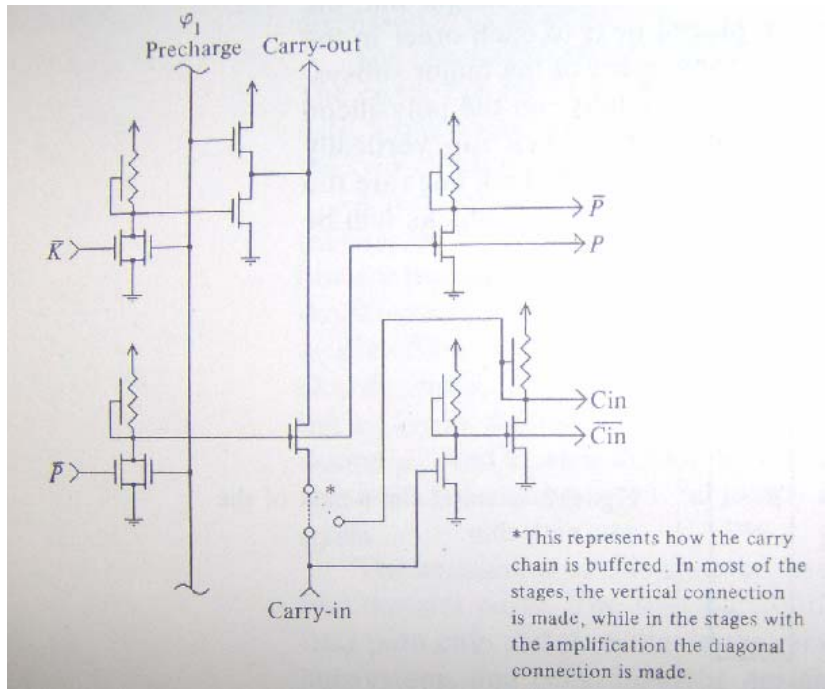


Fig.3. Lantul de transport de tip Manchester, al unitatii de executie

 


Fig.4. Reprezentarea abstracta a lantului de transport.

 


Fig. 5 Diagrama rețelei logice programabile, la nivelul tranzistoarelor de trecere,

 


Fig.6. Reprezentarea functională abstractă a rețelei logice programabile.

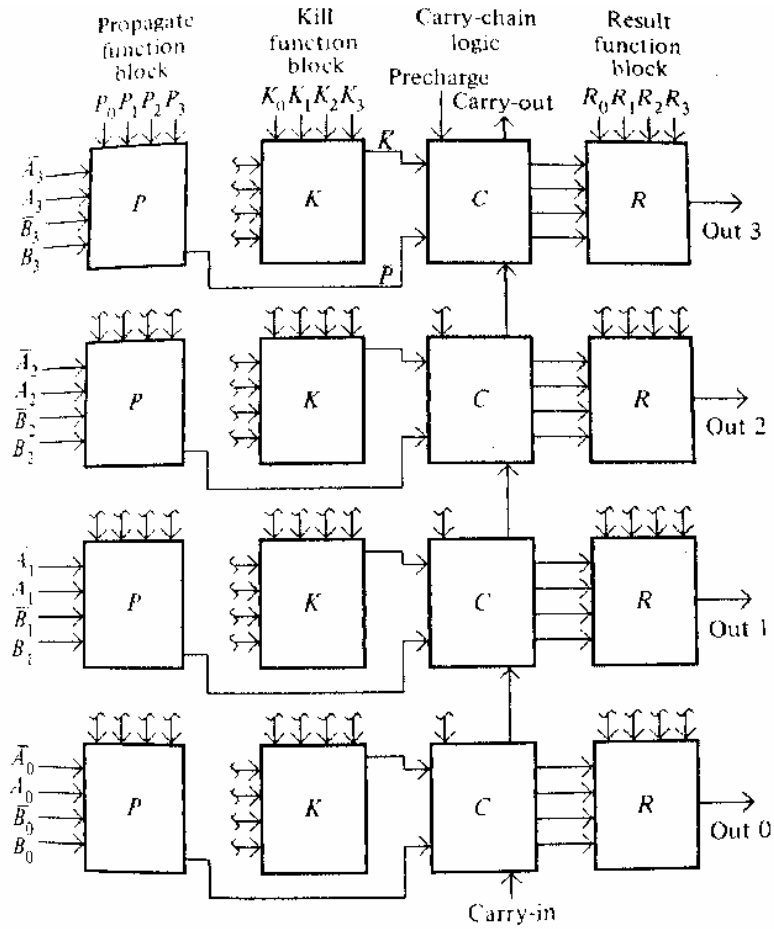


Fig.7. Schema bloc a unei UAL pe 4 biti

 


Fig.8. Circuit de comanda pentru UAL. Toate iesirile sunt la nivel ridicat pe durata lui  $\phi_2$  negat; termenii selectati sunt pe nivel coborât pe durata lui  $\phi_2$ ; codul de operatie este valid pe durata lui  $\phi_1$ .

 


Fig.9. Registru de intrare UAL si multiplexor.

 


Fig.10. Circuit de comanda pentru selectie . Toate iesirile sunt la nivel coborat pe durata lui  $\phi_1$ negat; termenii selectati sunt pe nivel ridicat pe durata lui  $\phi_1$ ; codul de operatie este valid pe durata lui  $\phi_2$ .

 


Fig.11. Registru de iesire.

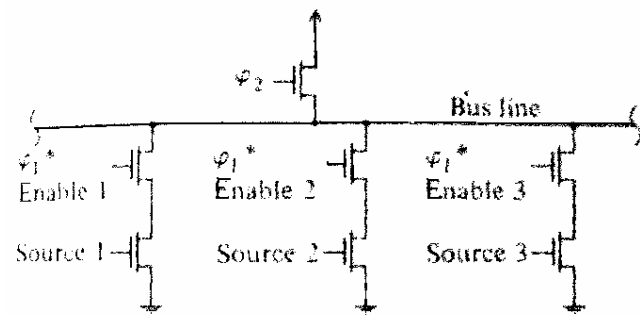


Fig.12. Circuit de magistrala preincarcata

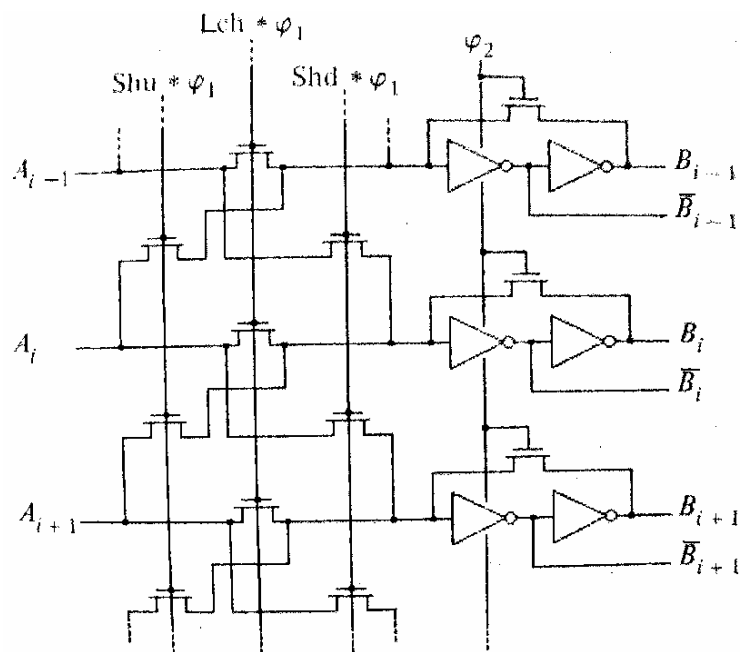


Fig. 13. Circuit simplu de deplasare cu un bit spre stanga.

 


Fig. 14. Comutator crossbar 4 x 4.

 


Fig. 15. Circuit de deplasare circulara (barrel shifter) 4 x 4.

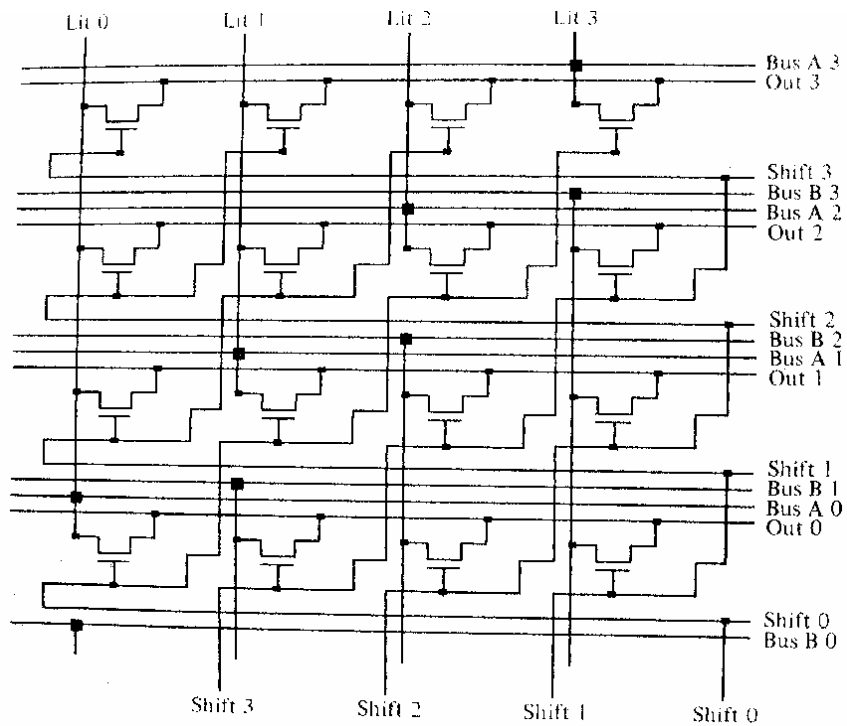


Fig. 16. Circuit de deplasare 4 x 4, cu trasee verticale sectionate si doua magistrale de date.

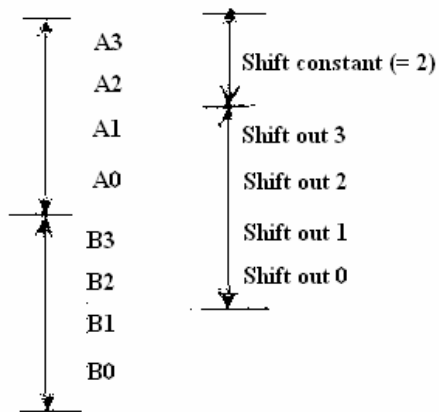


Fig . 17. Reprezentarea conceptuala a operarii circuitului de deplasare.



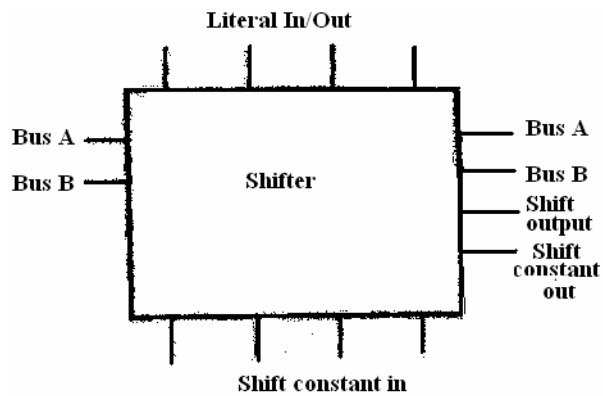


Fig. 18. Diagrama bloc a circuitului de deplasare.

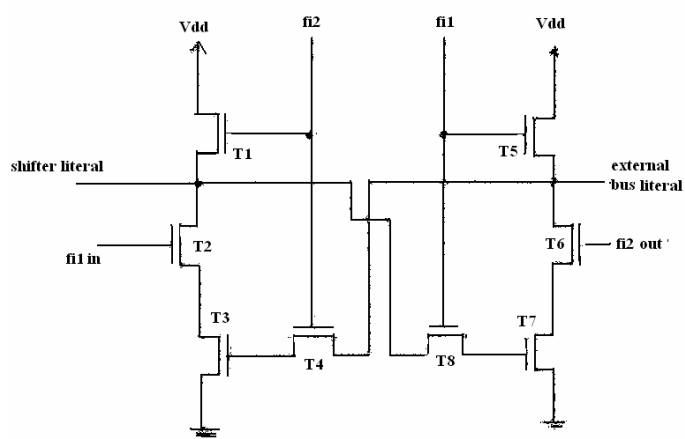


Fig. 19. Interfata Literal.

 


Fig. 20. Decodificator bazat pe NOR

 


Fig. 21. Decodificator bazat pe NAND

 


Fig. 22 Decodificator complementar.

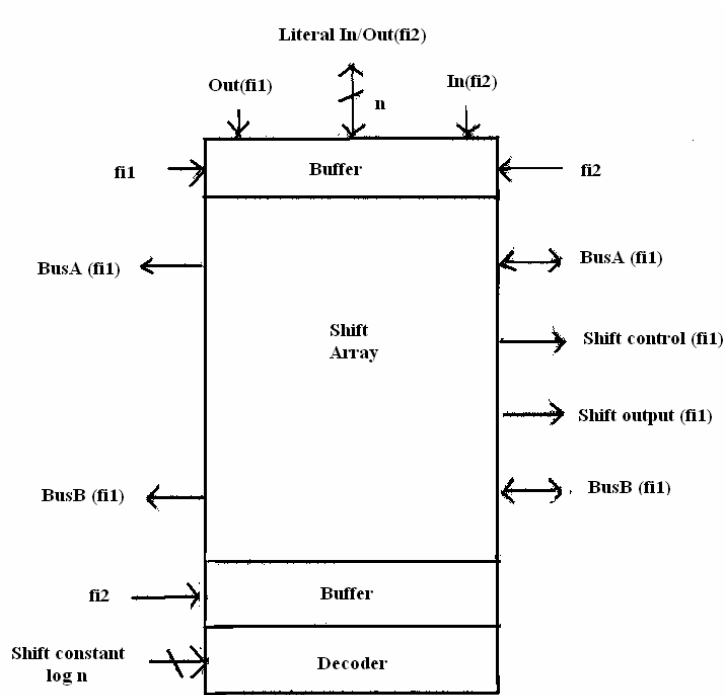


Fig. 23. Circuit de deplasare complet sincronizat.

 


Fig. 24 Celula de registru biport.

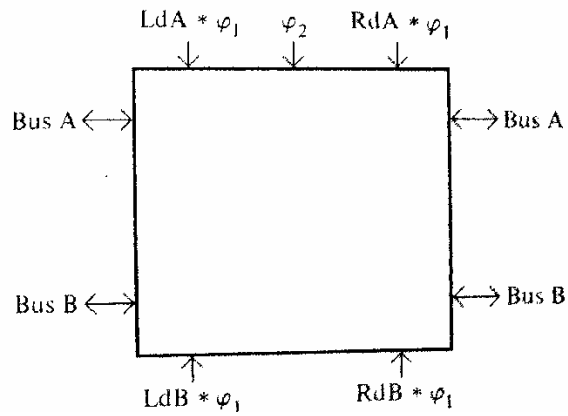


Fig. 25. Diagrama bloc a unei celule de registru biport.

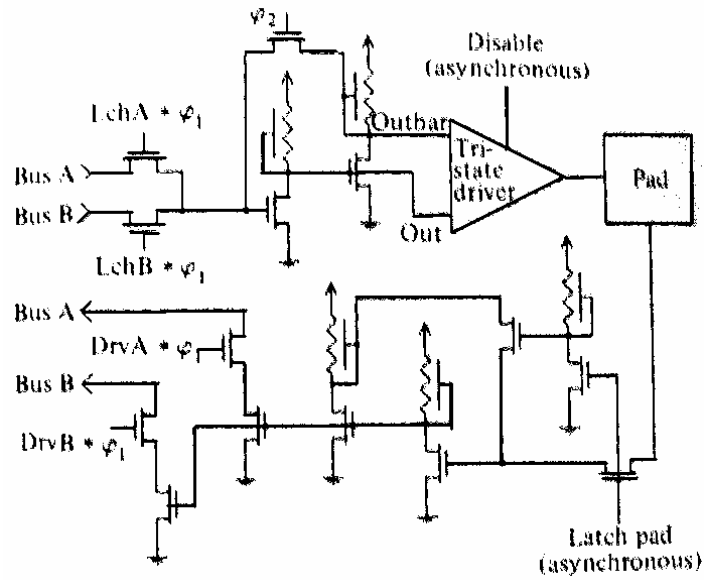


Fig. 26. Circuitul de I/E conectat la un plot bidirectional TS.

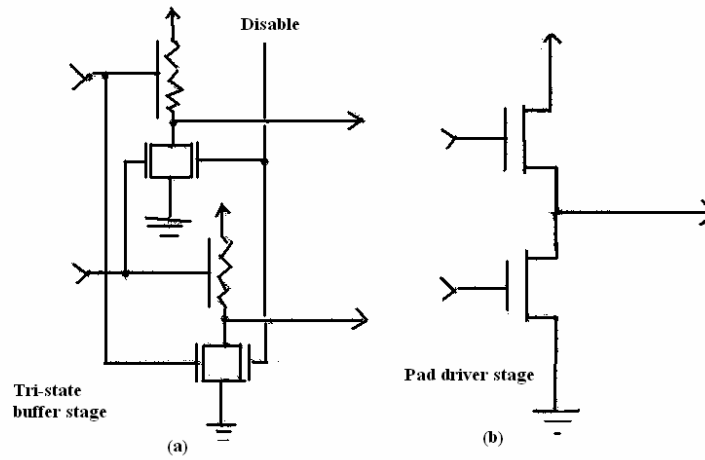


Fig. 28 Etaj tampon TS (a) si Circuit de comanda a plotului (b).

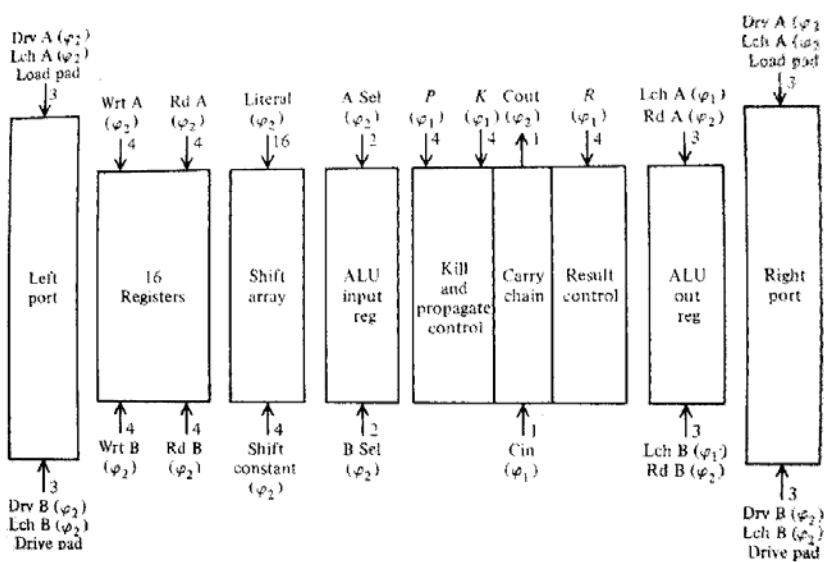


Fig. 29. Diagrama bloc a UAL, cu mentionarea traseelor de comanda.

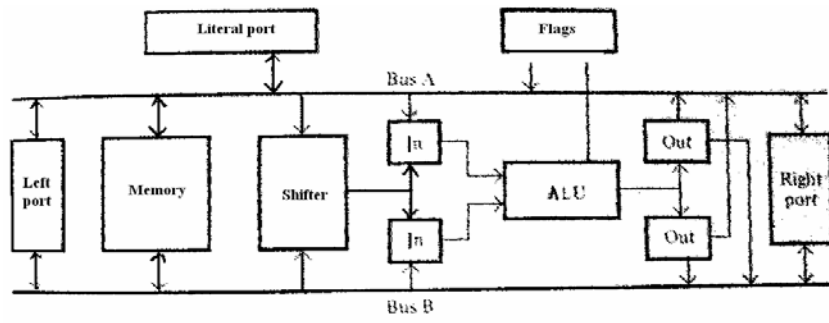


Fig. 30. Diagrama bloc a UAL.

 


Fig. 31. Operarea circuitului de deplasare.

 


Fig. 32. Diagrama bloc a unui bit al UAL.

 


Fig. 33 (a). Faza 2 COP (intra in  $\phi 1$ )

 


Fig. 33 (b). Faza 1 transfer COP de la Literal (intra in  $\phi 2$ )

 


Fig. 33 (c). Faza 1 COP normal (intra in  $\phi 2$ )

Tab. 1 Transferuri pe magistrale

	Bus A Source		Bus A Destination
0nnnn	Register <i>n</i>	0nnnn	Register <i>n</i>
10000	Right port pins	10000	Left port, drive now
10001	Right port latch	10001	Left port, drive <del>now</del>
10010	Left port pins	1001x	Left port, no drive
10011	Left port latch	10100	Right port, drive now
10100	ALU output latch A	10101	Right port, drive <del>now</del>
10101	ALU output latch B	1011x	Right port, no drive
10110	Flag register	11000	ALU input latch A
		11001	ALU input latch A gets shift out
		11010	ALU input latch A gets shift control
		11011	Flag register

Tab. 1 Transferuri pe magistrale

Bus B Source		Bus B Destination	
0nnnn	Register $n$	00nnnn	Register $n$
10000	Right port pins	010000	Left port, drive now
10001	Right port latch	010001	Left port, drive $\varphi_2$
10010	Left port pins	01001x	Left port, no drive
10011	Left port latch	010100	Right port, drive now
10100	ALU output latch $A$	010101	Right port, drive $\varphi_2$
10101	ALU output latch $B$	01011x	Right port, no drive
		0110xx	ALU input latch $B$
		10nnnn	ALU input latch $B$ gets shift output, shift constant $\neq n$
		11nnnn	ALU input latch $B$ gets shift control, shift constant $\neq n$

Tab2. Codificarea operatiilor in UAL, la nivelul microinstructiunilor.

	$K$	$P$	$R$	Cin	Cond	
$A + B$	1	6	6	0	0	Add
$A + B + Cin$	1	6	6	1	0	Add with carry
$A - B$	2	9	6	2	0	Subtract
$B - A$	4	9	6	2	0	Subtract reverse
$A - B - Cin$	2	9	6	1	0	Subtract with borrow
$B - A - Cin$	4	9	6	1	0	Subtract reverse with borrow
$\neg A$	12	3	6	2	0	Negative $A$
$\neg B$	10	5	6	2	0	Negative $B$
$A + 1$	3	12	6	2	0	Increment $A$
$B + 1$	5	10	6	2	0	Increment $B$
$A - 1$	12	3	9	2	0	Decrement $A$
$B - 1$	10	5	9	2	0	Decrement $B$
$A \wedge B$	0	8	12	0	0	Logical AND
$A \vee B$	0	14	12	0	0	Logical OR
$A \oplus B$	0	6	12	0	0	Logical EXOR
$\neg A$	0	3	12	0	0	Not $A$
$\neg B$	0	5	12	0	0	Not $B$
$A$	0	12	12	0	0	$A$
$B$	0	10	12	0	0	$B$
Mul	1	14	14	0	1	Multiply step
Div	3	15	15	0	2	Divide step
$A/O$	0	14	12	0	3	Conditional AND/OR
Mask	10	5	8	2	0	Generate mask
SHL $A$	3	0	10	0	0	Shift $A$ left
Zero	0	0	0	0	0	Zero

Tabela 3. Selectarea lui Cin

00	0
01	Flag bit
10	1
11	Flag bit complemented



Tab.4. Selectie OP Conditionala

Select	Flag bit	K	P	R	
0	x	----	----	----	Unconditional
1	0	---0	--0-	--0-	Multiply step
	1	----	0--	0--	
2	0	0--0	-00-	-00-	Divide step
	1	-00-	0--0	0--0	
3	0	----	----	----	AND/OR
	1	----	-00-	----	

Tab. 5. Selectarea noului bit indicator

Select	New flag bit
0	Old flag bit
1	Carry-out
2	MSB
3	Zero
4	Less than
5	Less than or equal
6	Higher (in absolute value)
7	Overflow





Tab. 6. Indicatorii de conditii.

Bit	Flag
0	Not changed
1	Not changed
2	Not changed
3	Not changed
4	Not changed
5	Previous value of flag bit
6	→ Carry into MSB stage
7	Less than or equal
8	→ Higher (in absolute value)
9	→ Less than
10	LSB
11	→ Zero
12	MSB
13	Overflow
14	→ Carry-out
15	Current flag bit

Tab. 7. Campul de memorare(latching)

Latching field	Register loaded
1xxx	Flag register loaded with current ALU flags
x1xx	ALU output latch A loaded with the ALU output
xx!x	ALU output latch B loaded with the ALU output
xxx!	The literal field during the next $\varphi_2$ is loaded with the contents of bus A during the last $\varphi_2$
0000	None of these registers are affected

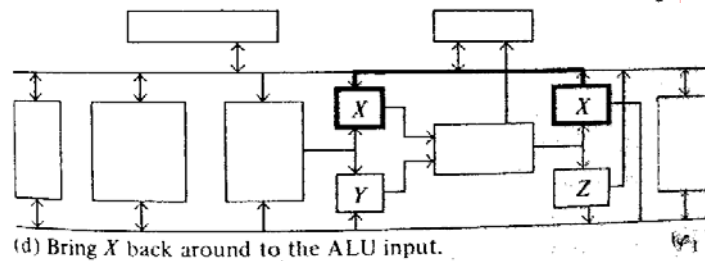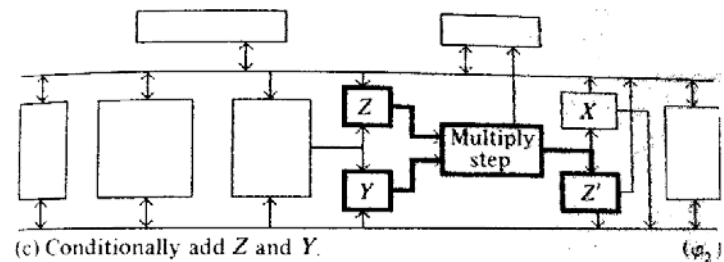 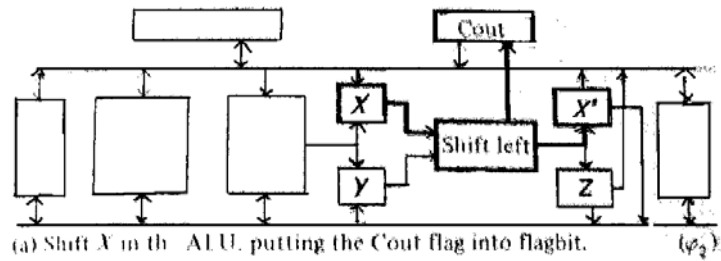Exemplu de microprogramare a inmultirii  $Z \leftarrow X \times Y$ , pe 16 biti.



- $\varphi_2$ : ALU.Out.A  $\leftarrow$  ALU(Shift A left)  $\leftarrow$  ALU.In.A;  
Latch Flags;
- $\varphi_1$ : ALU.In.A  $\leftarrow$  Shift.out, Bus.A  $\leftarrow$  ALU.Out.B;  
R[1]  $\leftarrow$  Bus.B  $\leftarrow$  R[0]; This gives a shift constant of 1.
- $\varphi_2$ : ALU.Out.B  $\leftarrow$  ALU(Multiply Step); *conditionally add.*  
Flag  $\leftarrow$  Cout;
- $\varphi_1$ : ALU.In.A  $\leftarrow$  Bus.A  $\leftarrow$  ALU.Out.A